


ELECTRONICS II

EXERCISE 2

1. In MOSFET the current control mechanism is based on an _____ established by the voltage applied to the control terminal.
 - (a) Electric field
 - (b) Induction layer
 - (c) Induced field
 - (d) None of the above
2. In the n-channel depletion-type MOSFET, the threshold voltage is
 - (a) The value of the Gate-to-source voltage at which the channel is completely depleted of electrons.
 - (b) The value of the Gate-to-source voltage at which a sufficient number of mobile electrons accumulate in the channel region to form a conducting channel.
 - (c) The value of the saturation voltage.
 - (d) The inversion layer voltage
3. What is an inversion layer?
 - (a) An induced channel
 - (b) A depletion layer
 - (c) A pn junction
 - (d) The gate electrode
4. For the JFET to operate in the pinch-off
 - (a) The drain voltage must be greater than the gate voltage by at least $|V_p|$.
 - (b) The source voltage must be greater than the drain voltage by $-V_p$.
 - (c) The gate voltage must be less than the source voltage by $-V_p$
 - (d) None of the above.
5. The conduction of the channel is proportional to
 - (a) The pn junction voltage between the source and the drain.
 - (b) The excess gate voltage
 - (c) The threshold voltage
 - (d) The inversion layer voltage
6. The maximum value of the gate-to-source voltage in an n-type JFET is
 - (a) -1 V
 - (b) $+1\text{ V}$
 - (c) 0 V
 - (d) 0.7 V


Give the names of the following circuit symbols.

7.

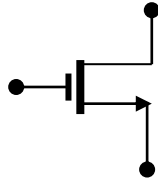


n-channel Enhancement MOSFET

8.

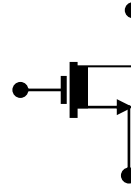


n-channel Depletion

9.

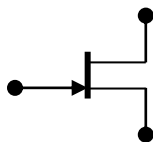


n-channel JFET

10.

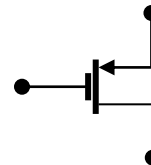


p-channel Enhancement MOSFET

11.

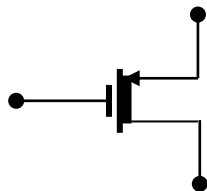

p-channel Depletion type MOSFET


12.

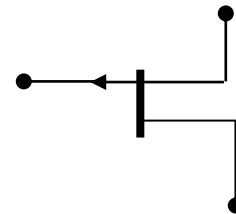

p-channel JFET

Example 1

Design the circuit of fig.1 so that the transistor operates at $I_D = 0.4\text{mA}$ and $V_D = +1\text{V}$. The NMOS transistor has $V_{t.} = 2\text{V}$, $\mu_n C_{ox} = 20\mu\text{A/V}^2$, $L = 10\text{ }\mu\text{m}$, and $W = 400\text{ }\mu\text{m}$. neglect the channel-length modulation effect (i.e. assume $\lambda = 0$).

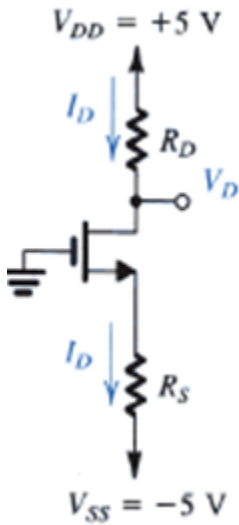

Example 2

Design the circuit in fig. 2 to obtain a current I_D of 0.4mA . give the value required for R and find the dc voltage V_D . Let the NMOS transistor have $V_{t.} = 2\text{ V}$, $\mu_n C_{ox} = 20\text{ }\mu\text{A/V}^2$, $L = 10\text{ }\mu\text{m}$, and $W = 100\text{ }\mu\text{m}$. neglect the channel-modulation effect (i.e. assume $\lambda = 0$).

