



CSM 153

CIRCUIT THEORY

Akwasi Acheampong Aning, PhD

COURSE OUTLINE

Unit 2: Direct Circuit Analysis

- a) Ohm's law
- b) Series and Parallel Circuits
- c) Methods of Analysis



www.knust.edu.gh

Ohm's Law

- **Electric current** flowing through a metallic conductor or wire is directly proportional to the **potential difference applied**, provided **temperature** and other **physical factors** remain constant. (i.e. $V \propto I$)
- Thus mathematical statement of the law is written as $V = IR$, where R is a constant defining resistance of the wire.
- This statement of Ohm's law is correct only in certain situations.



Ohm's Law

- The equation **defines resistance**, and it applies to all conducting devices, whether they obey Ohm's law or not.
- The importance of Ohm's law, however, is that a graph of V versus I is linear (straight line); that is R is independent of V .
- A **conducting material** obeys Ohm's law when the **resistivity** of the material is independent of the **magnitude** and **direction** of the applied electric field.



Ohm's Law

- Similarly, a **conducting device** obeys Ohm's law when the **resistance** of the device is independent of the **magnitude** and **polarity** of the applied potential difference.
- Therefore, all homogeneous materials (conductors, pure semiconductors or impure semiconductors) obey Ohm's law within some range of values of the electric field.
- However, if the electric field is too strong there are departures from Ohm's law in all cases.



Ohm's Law

- A conductor whose function in a circuit is to provide a **specific resistance** is called a **resistor**.
- Thus, resistor is a conductor with a specified resistance, which remains the same no matter what the magnitude and direction (polarity) of the applied potential difference may be.
- This means the resistance R of the device is independent of the magnitude and polarity of the potential difference.



Ohm's Law

- When potential difference V is applied to the ends of a wire and the current I through it is measured, the ratio of the p.d. V to the current I defines resistance R given by

$$R = V/I \text{ --- (8).}$$

- SI unit is the Volt per ampere or Ohm (Ω).

1



$$\Omega = 1VA^{-1}$$



Direct Circuit Analysis

Series and Parallel Circuits

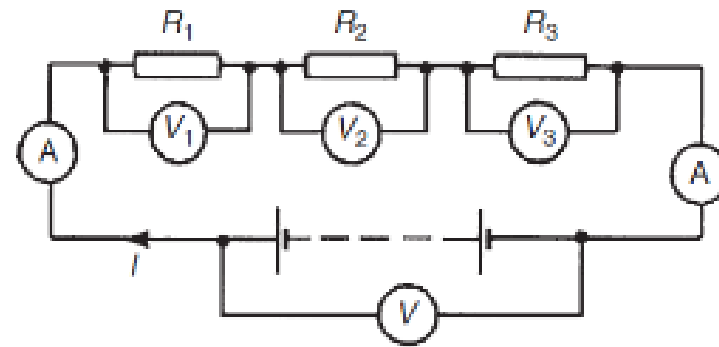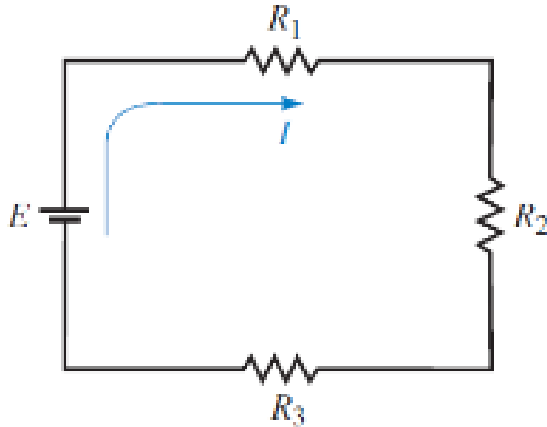- Two elements are said to be in series if they are connected at a single point and if there are no other current-carrying connections at this point



- The current I is the same in all parts of the circuit and hence the same reading is found on each of the two ammeters in the circuit
- The sum of the voltages V voltage V

Direct Circuit Analysis

Series and Parallel Circuits

From Ohm's law:

$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3 \text{ and } V = IR$$

where R is the total circuit resistance.

$$\text{Since } V = V_1 + V_2 + V_3$$

$$\text{then } IR = IR_1 + IR_2 + IR_3$$

Dividing throughout by I gives

$$R = R_1 + R_2 + R_3$$


Thus for a series circuit, the total resistance is obtained by adding together the values of the separate resistances.



Direct Circuit Analysis

Series and Parallel Circuits

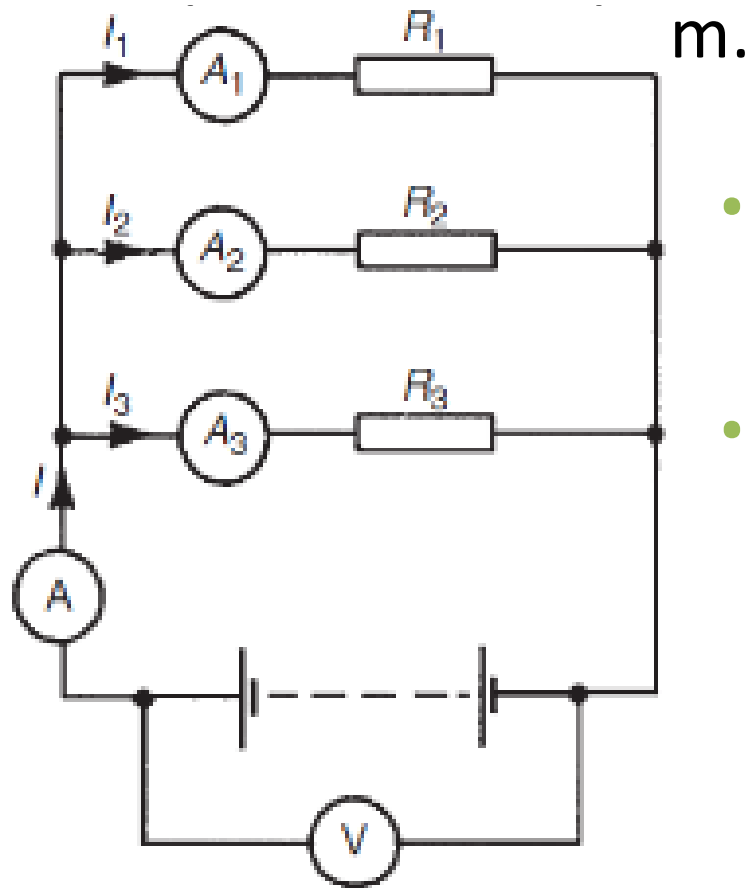- Elements or branches are said to be in a parallel connection when they have exactly two nodes in common. Additionally, these parallel elements or branches will have the same



- The sum of the currents I_1 , I_2 , and I_3 is equal to the current I
- The source potential difference (pd) is the same across each of the resistors



www.knust.edu.gh

Direct Circuit Analysis

Series and Parallel Circuits

From Ohm's law:

$$I_1 = V/R_1, I_2 = V/R_2, I_3 = V/R_3 \text{ and } I = V/R$$

where R is the total resistance of the circuit

Since $I = I_1 + I_2 + I_3$

$$\text{then } V/R = V/R_1 + V/R_2 + V/R_3$$

Dividing throughout by V gives

$$1/R = 1/R_1 + 1/R_2 + 1/R_3$$



Direct Circuit Analysis

Series and Parallel Circuits

The total resistance R for a parallel circuit is:

$$1/R = 1/R_1 + 1/R_2 + 1/R_3$$

For a special case of 2 resistors in parallel

$$1/R = 1/R_1 + 1/R_2 = \frac{R_2 + R_1}{R_1 R_2}$$

$$\text{Hence } R = \frac{R_2 R_1}{R_1 + R_2}$$



Direct Circuit Analysis

Series and Parallel Circuits

Node: A point at which two or more elements have a common connection called a node

Branch: A single path in a network composed of one simple element and the node at each end of that element

Loop: A simple closed path in a circuit in which no circuit element or node is encountered more than once



www.knust.edu.gh

Direct Circuit Analysis

Series and Parallel Circuits

- Electrical network is usually regarded to be a complicated (complex) system of electrical conductors.
- In dealing with such networks the Ohm's law was extended to the networks by a German physicist Gustav R. Kirchhoff (1847) in the form of two laws.

However, it must be emphasized that:

- 1) The laws enabled the **current in any part** of an electrical network to be calculated.
- 2) All circuits can be solved by Kirchhoff's laws because they **do not depend on series or parallel** connection of resistors/ conductors.



www.knust.edu.gh


Direct Circuit Analysis

Series and Parallel Circuits

Kirchoff's Law 1

- The total current flowing into a junction in a circuit (electrical network) is equal to the total current flowing out of (leaving) the junction.
- The algebraic sum of currents directed in and out at a junction of a circuit must be zero.

i.e. 

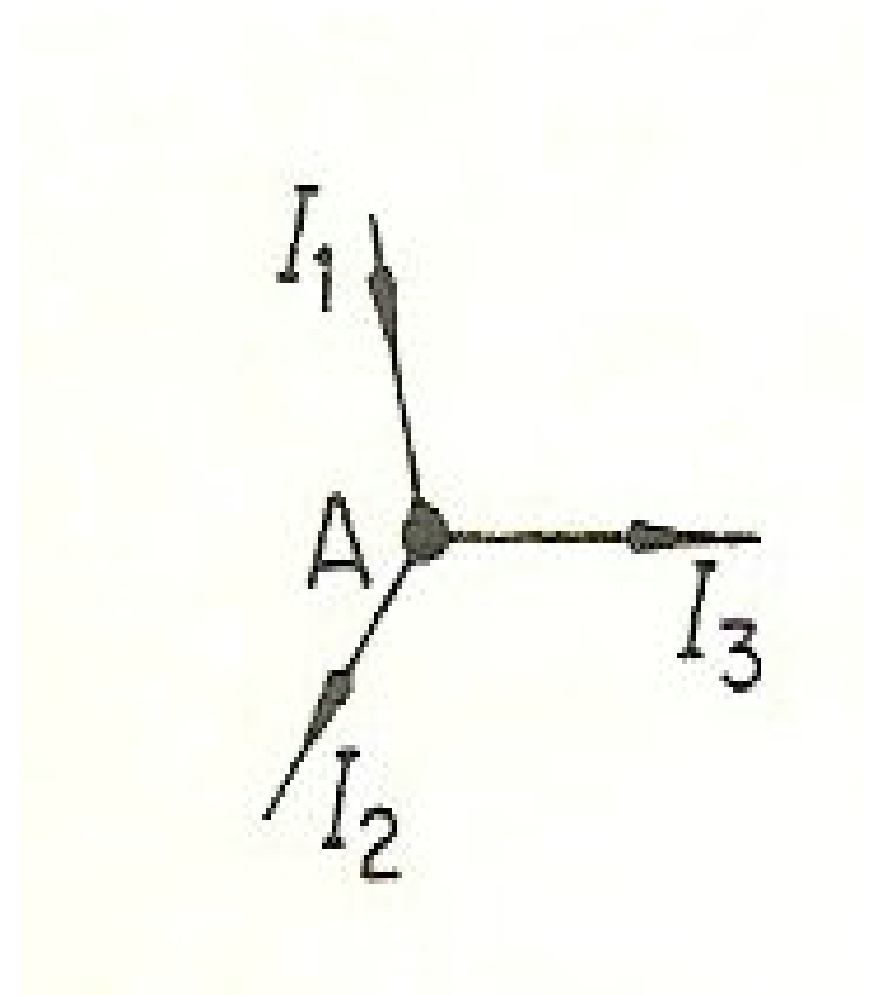

Direct Circuit Analysis

Series and Parallel Circuits

Kirchoff's Law 1

The first law applies to any point or junction in an electrical network.

If currents flowing in and out of the junction flows for a time t seconds, then we have



This means total charge flowing to the junction is equal to total charge flowing out of it.



Direct Circuit Analysis

Series and Parallel Circuits

Kirchoff's Law 1

- This implies there is neither a build up (accumulation or pile up) nor a depletion of charge at a junction.
- Therefore, the first law is a statement of the conservation of charge for a steady flow of charge or current.
- This is because charge is neither created nor destroyed, but can be transferred from one point to another.
- The law is often put in the form: *The algebraic sum of currents directed in and out at a junction of a circuit must be zero* .

$$\sum I = 0, \quad \text{i.e. } I$$




www.knust.edu.gh

Direct Circuit Analysis

Series and Parallel Circuits

Kirchoff's Law 2

□ Round a closed loop (path) the algebraic sum of the emfs is equal to the algebraic sum of the voltage (pd) drops. i.

$$\text{e. } \sum E = \sum IR$$




Direct Circuit Analysis

Series and Parallel Circuits

Current and Voltage Divider Rules

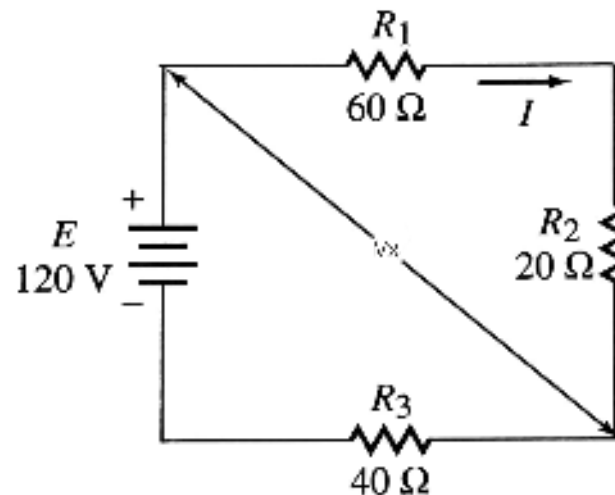- **Voltage Divider Rule:** The voltage across a part of a series circuit is equal to the resistance of the part multiplied by the total voltage and divided by the equivalent resistance
- Voltage division allows us to calculate what fraction of the total voltage across a series string of resistors is dropped across any one resistor (or group of resistors)



- $$V_x = \frac{R_x}{R_{eq}} V$$




Direct Circuit Analysis

Series and Parallel Circuits

Current and Voltage Divider Rules

- **Current Divider Rule:** The current in a branch of a parallel circuit is equal to the current entering the circuit multiplied by the equivalent resistance of the branches divided by the resistance in the branch
- Current division allows us to calculate what fraction of the total current into a parallel string of resistors flows through any one of the resistors

- $$I_x = \frac{R_{eq}}{R_x} I_T$$

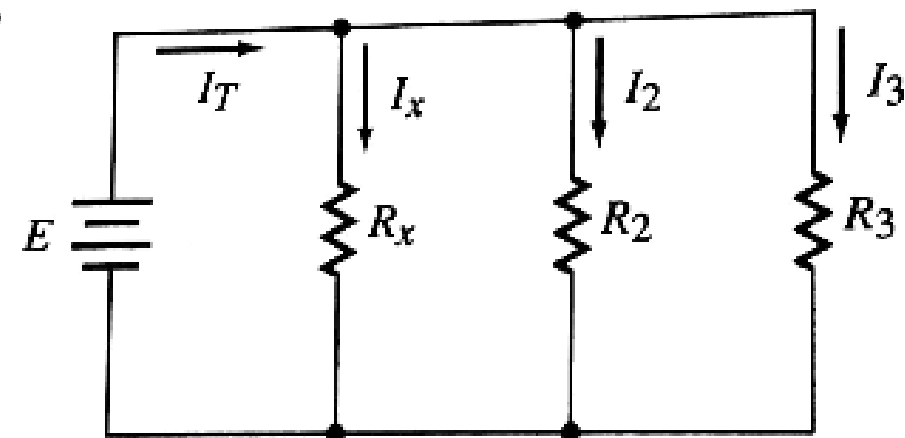


www.knust.edu.gh

Direct Circuit Analysis

Series and Parallel Circuits

Current and Voltage Divider Rules

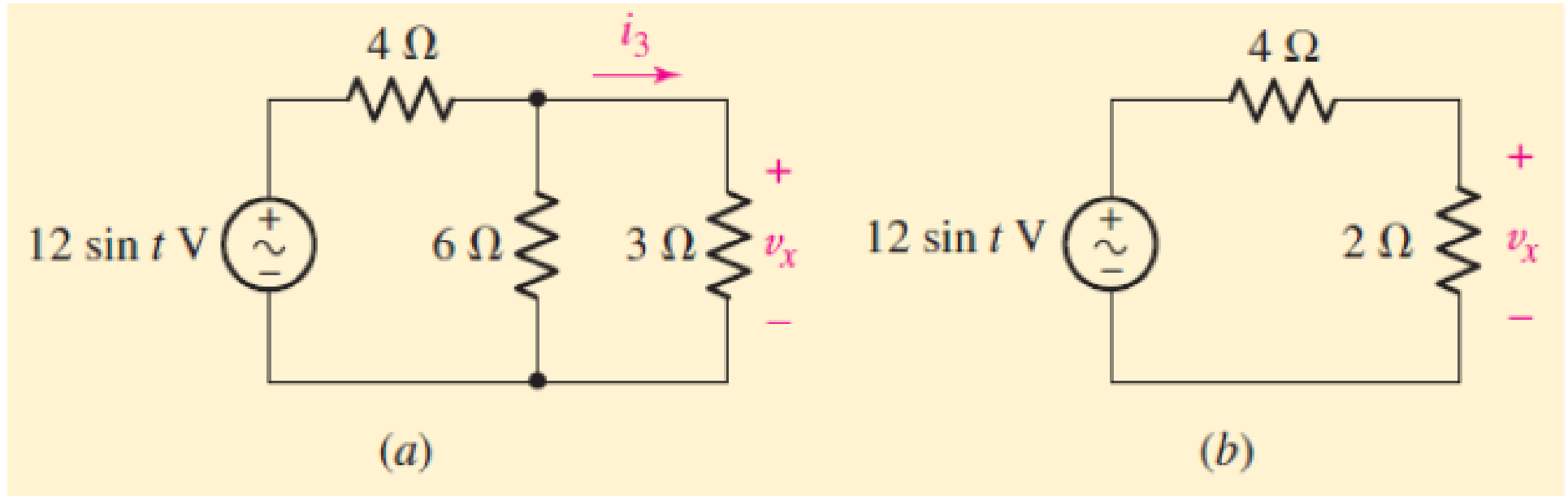

- Calculate the voltage V_x .

Soln


- $$V_x = 12 \sin t \frac{2}{4+2} = 4 \sin t \text{ V}$$



Direct Circuit Analysis

Series and Parallel Circuits

Current and Voltage Divider Rules

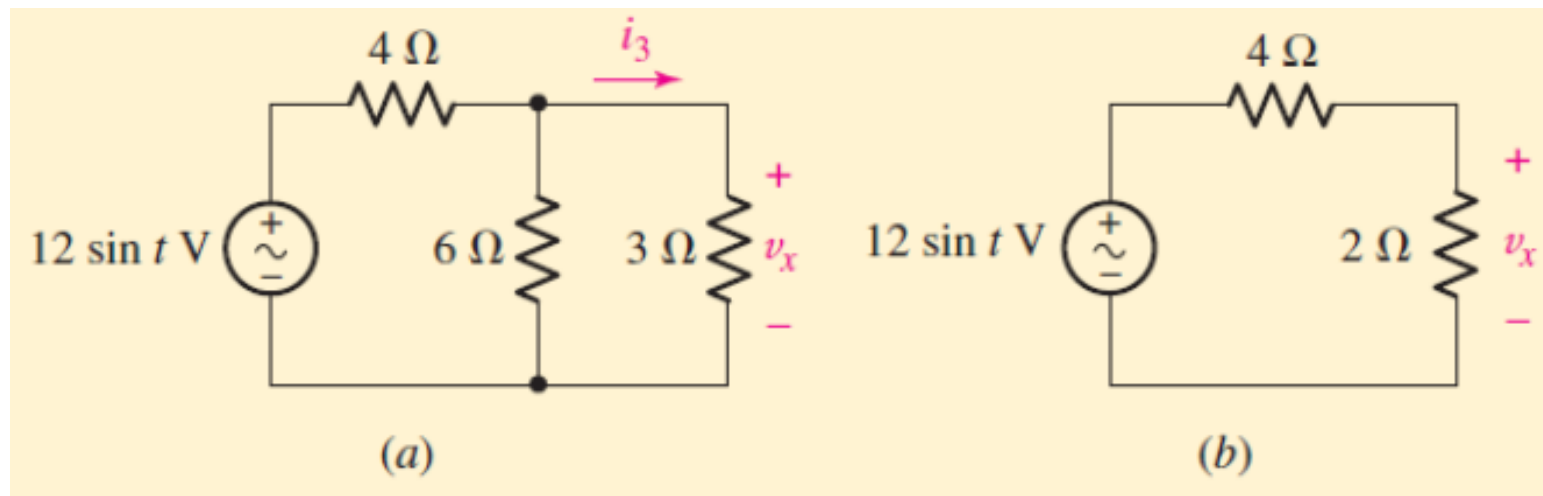

- Calculate the voltage the current through the 3Ω .

Soln

$$i(t) = \frac{12 \sin t}{4 + 3 || 6} = \frac{12 \sin t}{4 + 2} = 2 \sin t \text{ A} \quad \dots \text{ (total current in cct)}$$

$$i_3(t) = 2 \sin t \frac{6}{6 + 3} = \frac{4}{3} \sin t \text{ A}$$



Direct Circuit Analysis

Series and Parallel Circuits

Nodal analysis

- Choose one node as the reference node. Then label the node voltages v measured with respect to the reference node
- If the circuit contains only current sources, apply KCL at each nonreference node

Mesh analysis


- First make certain that the network is a planar network.
- Assign a clockwise mesh current in each mesh: i
- If the circuit contains only voltage sources, apply KVL around each mesh



Direct Circuit Analysis

Series and Parallel Circuits

Circuit Analysis

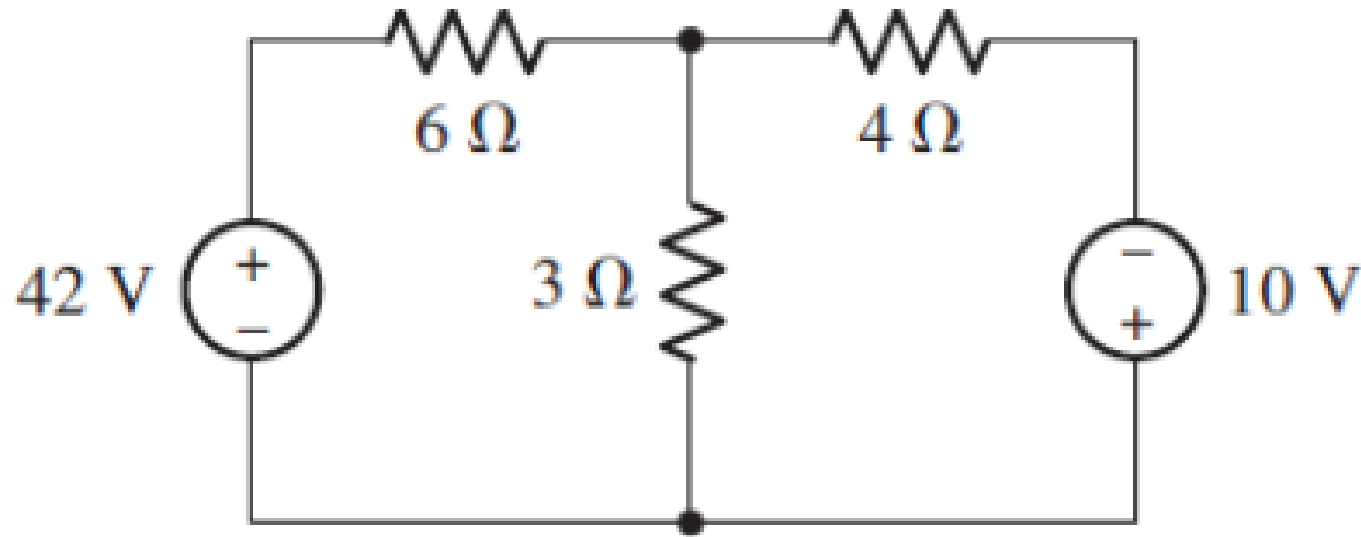

Find


- i. the current in each resistor
- ii. the voltage across each resistor



Direct Circuit Analysis

Series and Parallel Circuits

Circuit Analysis

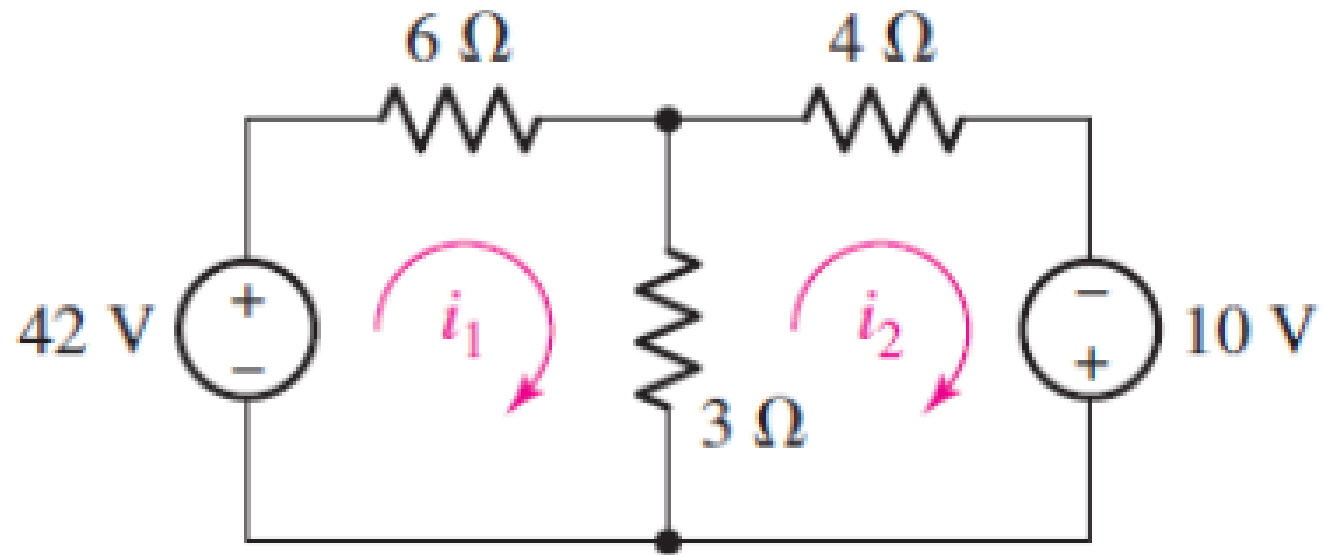

For mesh 1: $-42 + 6i + 3(i_1 - i_2) = 0$

For mesh 2: $-10 + 3(i_2 - i_1) + 4i_2 = 0$

$i_1 = 6 \text{ A},$ $i_2 = 4 \text{ A}$ and current the 3Ω is
 $i_1 - i_2 = 2 \text{ A}$


Direct Circuit Analysis

Series and Parallel Circuits

Circuit Analysis

- Determine the current I_x

Soln

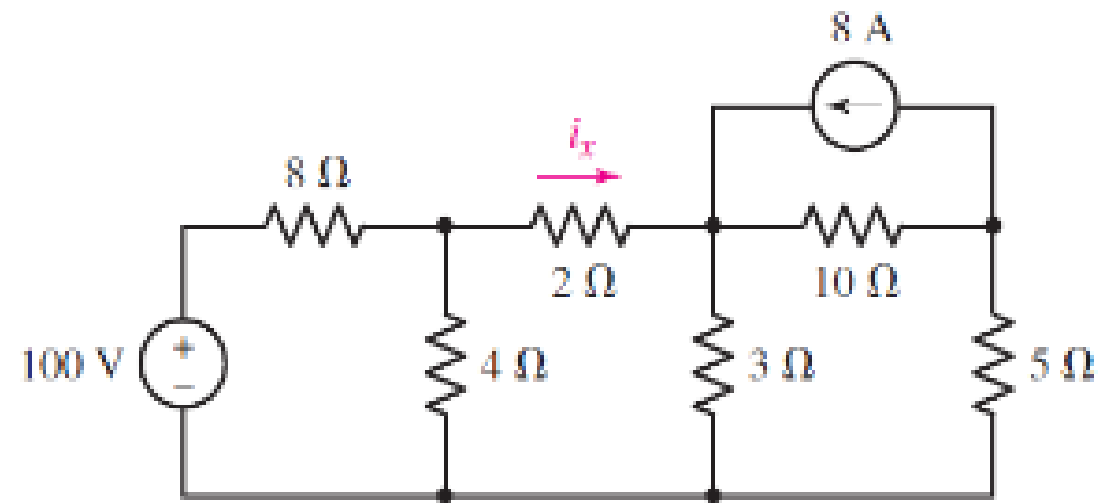


$$-100 + 8i_1 + 4(i_1 - i_2) = 0 \quad \text{or} \quad 12i_1 - 4i_2 = 100$$

$$4(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0 \quad \text{or} \quad -4i_1 + 9i_2 - 3i_3 = 0$$

$$3(i_3 - i_2) + 10(i_3 + 8) + 5i_3 = 0 \quad \text{or} \quad -3i_2 + 18i_3 = -80$$

- $i_x = i_2 = 2.79 \text{ A}$

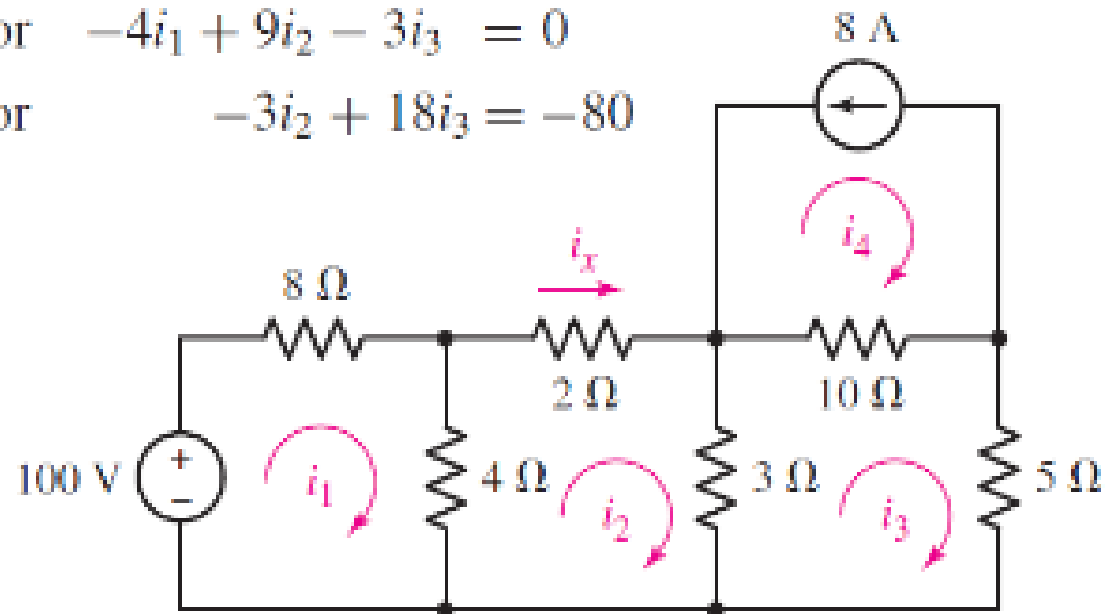



www.knust.edu.gh

Direct Circuit Analysis

Series and Parallel Circuits

Circuit Analysis

- Find the mesh currents

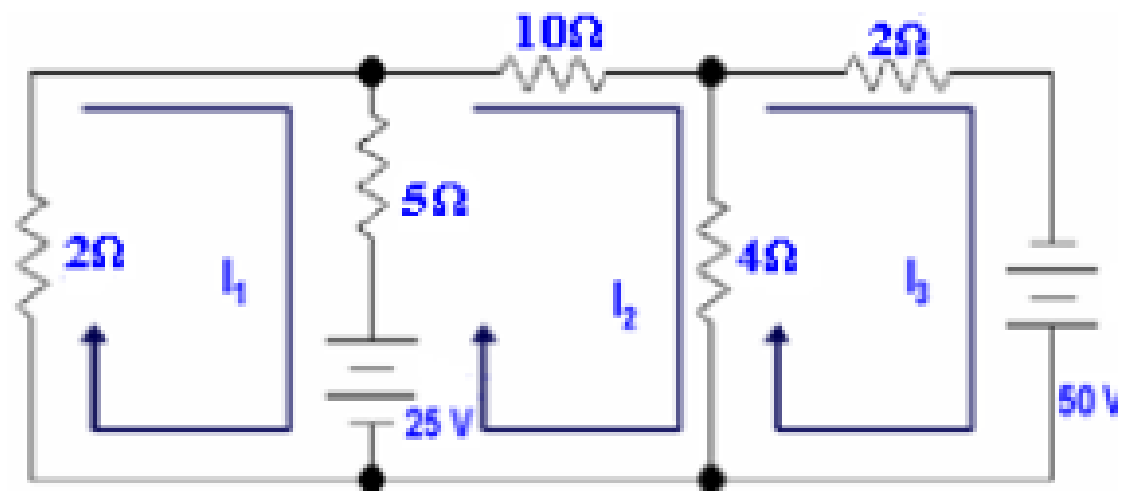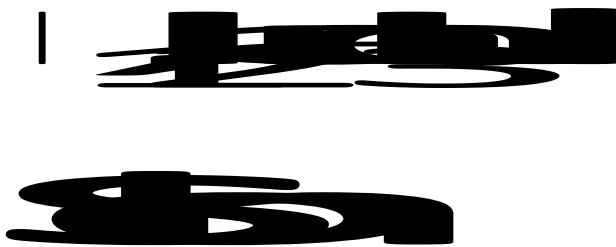

KVL equation for loop 1

$$2I_1 + 5(I_1 - I_2) = -25$$

$$2I_1 + 5I_1 - 5I_2 = -25$$

$$7I_1 - 5I_2 = -25$$

KVL equation for loop 2

$$10I_2 + 4(I_2 - I_3) + 5(I_2 - I_1) = 25$$

$$10I_2 + 4I_2 - 4I_3 + 5I_2 - 5I_1 = 25$$

$$-5I_1 + 19I_2 - 4I_3 = 25$$

KVL equation for loop 3

$$2I_3 + 4(I_3 - I_2) = 50$$

$$2I_3 + 4I_3 - 4I_2 = 50$$

$$-4I_2 + 6I_3 = 50$$



www.knust.edu.gh

Direct Circuit Analysis

Series and Parallel Circuits

Circuit Analysis



We will write equation A ,B and C In matrix form

$$\begin{bmatrix} 7 & -5 & 0 \\ -5 & 19 & -4 \\ 0 & -4 & 6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -25 \\ 25 \\ 50 \end{bmatrix}$$

The determinant of the coefficient matrix is

$$|A| = \begin{vmatrix} 7 & -5 & 0 \\ -5 & 19 & -4 \\ 0 & -4 & 6 \end{vmatrix}$$

$$|A| = 536$$

By Cramer's rule

$$I_1 = \frac{\begin{vmatrix} -25 & -5 & 0 \\ 25 & 19 & -4 \\ 50 & -4 & 6 \end{vmatrix}}{\begin{vmatrix} 7 & -5 & 0 \\ -5 & 19 & -4 \\ 0 & -4 & 6 \end{vmatrix}}$$

$$I_1 = (-700) \div 536$$

$$I_1 = -1.31 \text{ A}$$




www.knust.edu.gh

Direct Circuit Analysis

Series and Parallel Circuits

Circuit Analysis

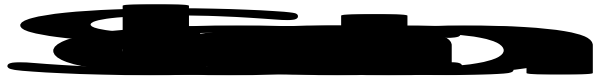

$$I_2 = \begin{vmatrix} 7 & -25 & 0 \\ -5 & 25 & -4 \\ 0 & 50 & 6 \end{vmatrix} \div \begin{vmatrix} 7 & -5 & 0 \\ -5 & 19 & -4 \\ 0 & -4 & 6 \end{vmatrix}$$

$$I_2 = 1700/536$$

$$I_2 = 3.17 \text{ A}$$

$$I_3 = \begin{vmatrix} 7 & -5 & -25 \\ -5 & 19 & 25 \\ 0 & -4 & 50 \end{vmatrix} \div \begin{vmatrix} 7 & -5 & 0 \\ -5 & 19 & -4 \\ 0 & -4 & 6 \end{vmatrix}$$

$$I_3 = 5600/536$$

$$I_3 = 10.45 \text{ A}$$



Cramer's Rule

The solution of the system of equations


$$\begin{aligned}a_1x + b_1y + c_1z &= d_1 \\a_2x + b_2y + c_2z &= d_2 \\a_3x + b_3y + c_3z &= d_3\end{aligned}$$

is given by $x = \frac{D_x}{D}$, $y = \frac{D_y}{D}$, and $z = \frac{D_z}{D}$, where

$$D = \begin{vmatrix} a_1 & b_1 & c_1 \\ a_2 & b_2 & c_2 \\ a_3 & b_3 & c_3 \end{vmatrix}, \quad D_x = \begin{vmatrix} d_1 & b_1 & c_1 \\ d_2 & b_2 & c_2 \\ d_3 & b_3 & c_3 \end{vmatrix}, \quad D_y = \begin{vmatrix} a_1 & d_1 & c_1 \\ a_2 & d_2 & c_2 \\ a_3 & d_3 & c_3 \end{vmatrix}, \quad D_z = \begin{vmatrix} a_1 & b_1 & d_1 \\ a_2 & b_2 & d_2 \\ a_3 & b_3 & d_3 \end{vmatrix}, \text{ and } D \neq 0.$$



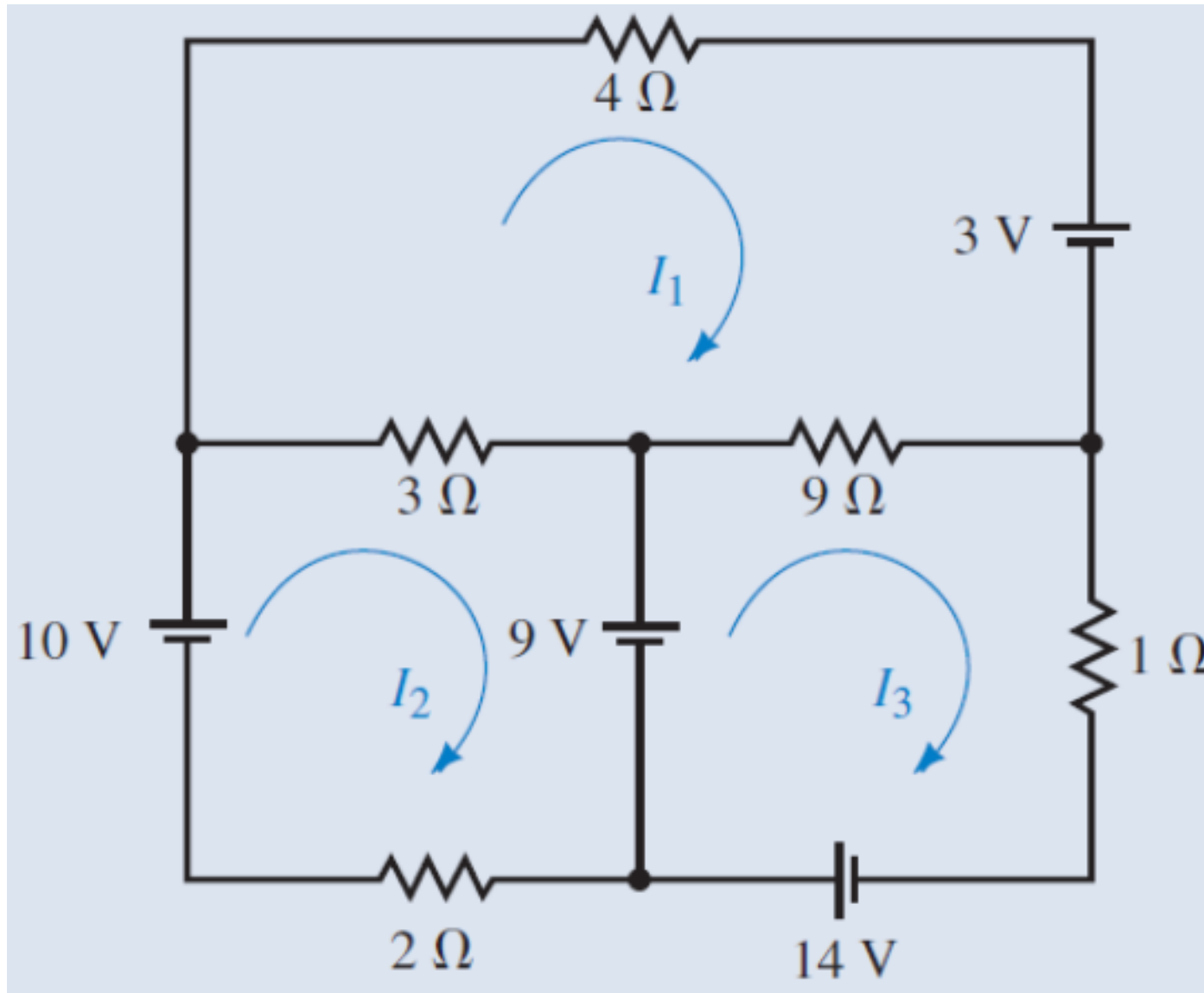Use the mesh analysis to find the loop currents



Merci



www.knust.edu.gh